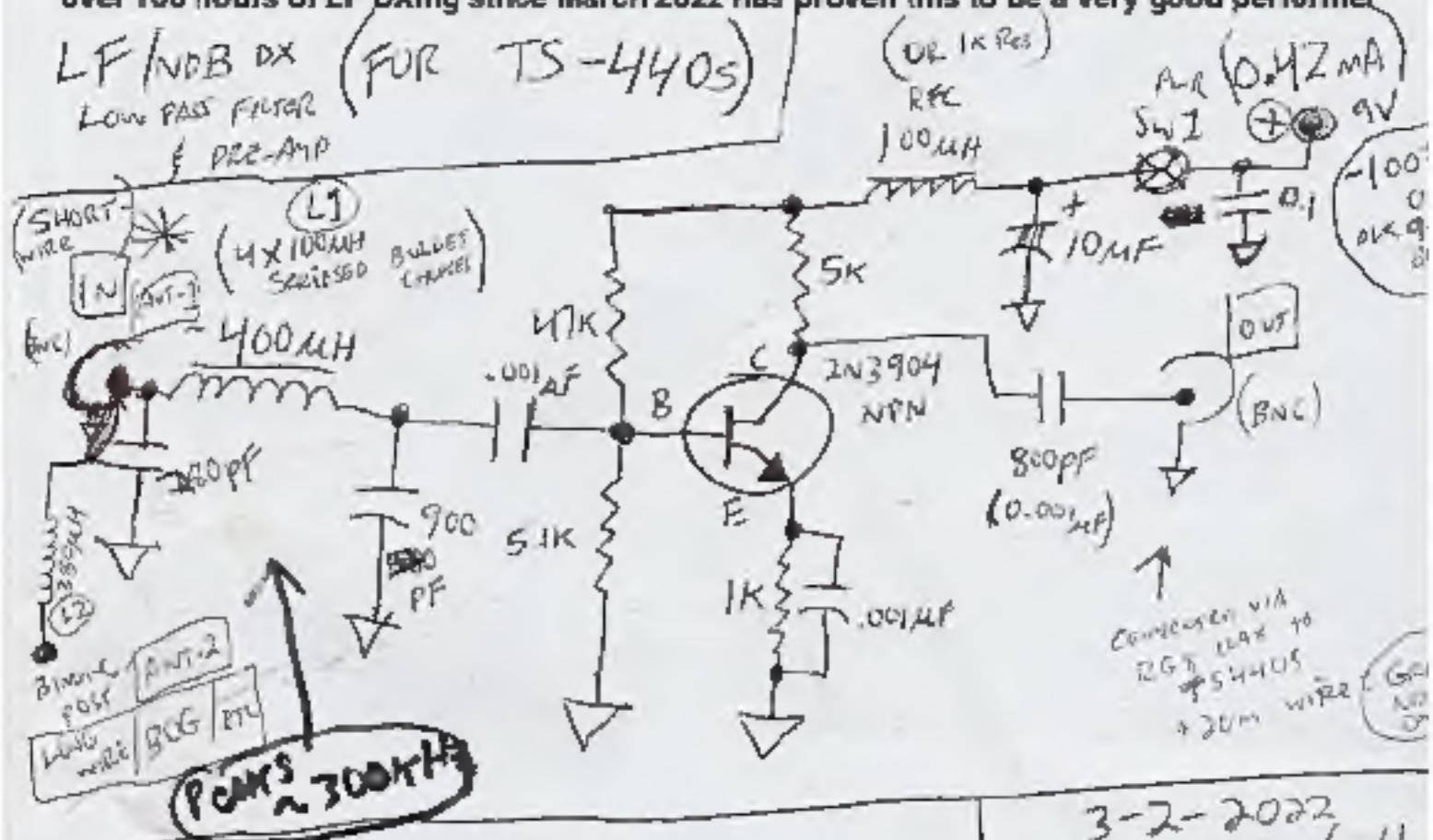


over 100 hours of LF DXing since March 2022 has proven this to be a very good performer

## LF / NOB DX (FOR TS-440S)

LOW PASS FILTER  
& PZC-AMP



IN = 15m m/w. vee +  
ANT. 1 10M OF RG-8

COAX FEED TO

INPUT. = "SHORT WIRE" ANTENNA

3-2-2022  
TESTED AND (Dx!!)

- N6NKS -

Sept 2022

- UPDATES 14 Sept 2022

"A QUICK BUT GOOD FIX

TO BE ABLE TO NOB DX ON MY HAM STN. SET-UP!  
(KNWD TS440S op) (NO B6B D1D)



LF LOWPASS  
FLUKE WIRE

YAESU FET-7700

LF LOWPASS  
FILTER

IN

210uH

270uH

OUT

800  
PF

1200  
PF

800  
PF

TWO ALNT ALTERNATIVE  
LF LOW PASS  
FILTERS IN  
LOCATIONS  
(m)  
w/ HIGHER AM B2B  
FIELD STRENGTHS  
(local sites)

